

EXP NO: 8

CARRY LOOK-AHEAD ADDER

DATE:

08/11/22

AIM:

To design and implement carry look-ahead adder.

COMPONENTS REQUIRED:


S-NO	NAME OF COMPONENTS	SPECIFICATION	QUANTITY
1	AND gate	IC 7408	1
2	X-OR gate	IC 7402	1
3	OR gate	IC 7432	1
4	Digital trainer kit	-	1
5	Connecting wires	-	As required

PROCEDURE :

- * Connections are given as per the truth circuit diagram
- * Logical input are given as circuit diagram
- * Observe the output and verify the truth table.



LOGIC DIAGRAM:

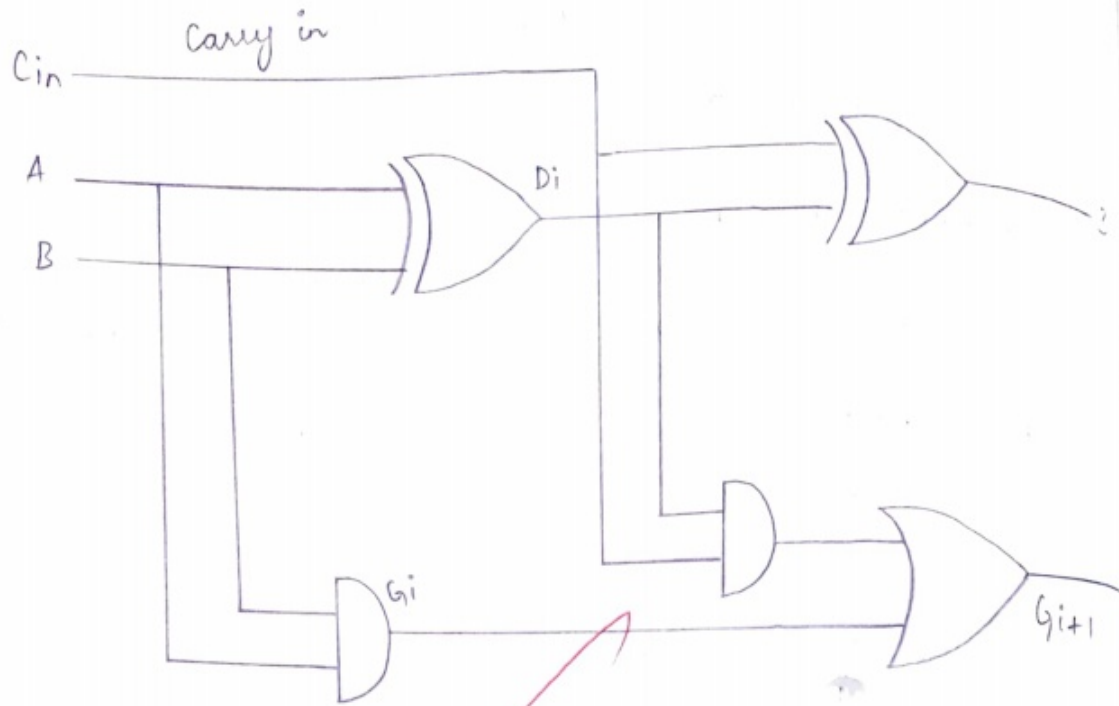

TRUTH TABLE:

A	B	C_i	C_{i+1}	Condition
0	0	0	0	No carry generate
0	0	1	0	
0	1	0	0	
0	1	1	1	No carry propagate
1	0	0	0	
1	0	1	1	
1	1	0	1	carry
1	1	1	1	generate

RESULT:

The carry look ahead adder is designed and implemented successfully.

@