

HARTLEY AND COLPITT'S OSCILLATOR.AIM:

To design and construct the Hartley and Colpitt's oscillator and verify its theoretical and practical frequencies.


COMPONENTS REQUIRED:

Sl. No.	components	Range	Quantity
1.	Transistor	BC 107	1
2.	Resistor	22K Ω , 2.2K Ω 4.5K Ω , 330 Ω	Each 1
3.	capacitors	0.1 μ F 10 μ F	1 1
4.	Decade Inductance box	-	1


APPARATUS REQUIRED:

Sl. No.	apparatus	Range	Quantity
1.	R.P.S	(0-30)V	1
2.	signal Generator	(0-2)MHz	1
3.	CRO	(0-30)MHz	1

COLPITT'S OSCILLATOR:

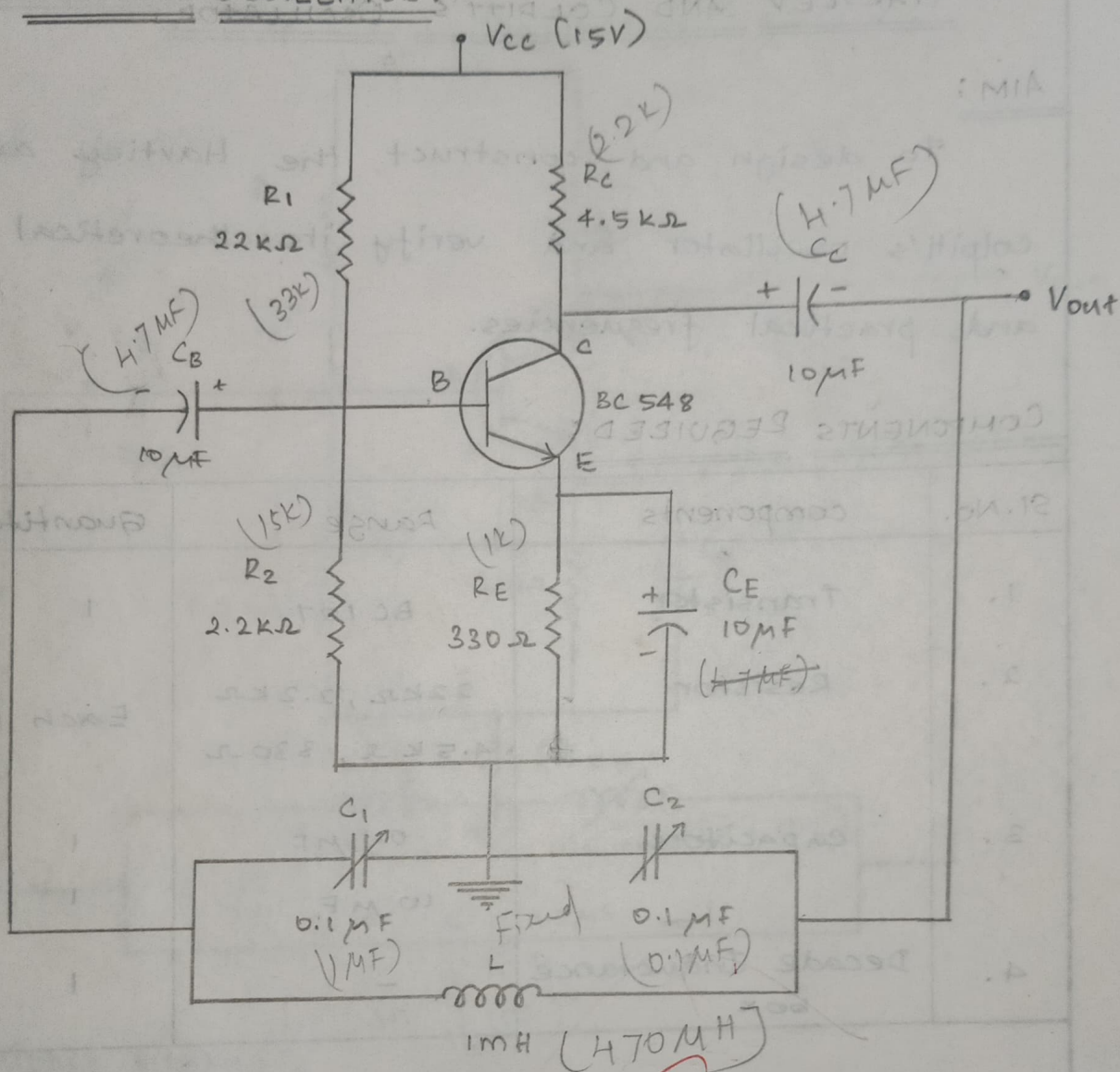

MODEL GRAPH:

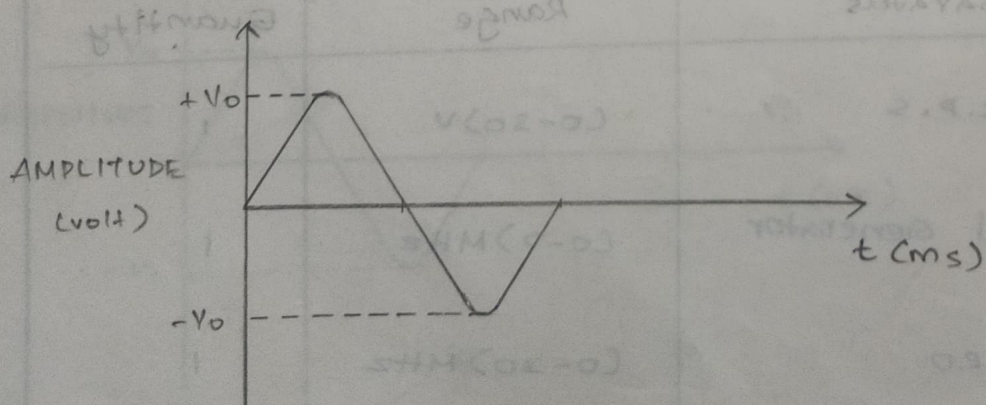

FORMULA :

$$i) I_B = \frac{I_C}{\beta}$$

$$ii) R_C = \frac{V_{CC} - V_{CE}}{I_C} - R_E \quad V_{CC} - V_{CE} = I_C R_C + I_E R_E$$

$$iii) I_E = I_B + I_C$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$iv) V_{TH} = I_B R_B + V_{BE} + I_E R_E$$

$$v) R_{TH} = \frac{(1-\beta)(1+\beta)}{(1-\beta-\beta)} \cdot R_E$$

$$vi) R_1 = \frac{V_{CC}}{V_{TH}} \cdot R_{TH}$$

$$vii) R_2 = \frac{V_{TH}}{V_{CC} - V_{TH}} \cdot R_1$$

HARTLEY OSCILLATOR :

$$L_{eq} = L_1 + L_2$$

$$f = \frac{1}{2\pi \sqrt{L_{eq} \cdot C}}$$

COLDPITT'S OSCILLATOR :

$$C_{eq} = \frac{C_1 \cdot C_2}{C_1 + C_2}$$

$$f = \frac{1}{2\pi \sqrt{L \cdot C_{eq}}}$$

COLPITT'S OSCILLATOR:

S. No.	WAVEFORM	AMPLITUDE (V)	TIME (ms)	FREQUENCY (Hz)
1.	Output signal	$2.6 \times 10V$	$24.34 \mu s$ $1 \times 20 \mu s$	25 kHz 50 kHz

24 kHz

THEORY

COLPITT'S OSCILLATOR:

Colpitt's oscillator is same as that of the Hartley oscillator except that the emitter is connected between the capacitance C_1 and C_2 . The resistors R_1 , R_2 and E_{ie} provides the necessary biasing conditions. The functions of C_c is to block d.c. current and to provide an a.c. path. The radio frequency choke offers very high impedance to high frequency current. Thus it prevents radio frequency current from reaching the collector.

The ~~frequency~~ determining network is a parallel combination resonant circuit consisting of capacitor C_1 and C_2 and inductor L . The voltage developed across C_1 provides the regenerative feedback required for the sustained oscillations. When the collector supply voltage is switched ON, transient current is produced in the tank circuit.

COLDWELL'S OSCILLATOR:

$$L = 200 \mu H$$

$$C_1 = 0.1 \mu F$$

$$C_2 = 0.1 \mu F$$

$$C_{eq} = \frac{0.1 \times 0.1 \times 10^{-12}}{0.2 \times 10^{-6}} = 5 \times 10^{-8}$$

$$f = \frac{1}{2\pi \sqrt{L \cdot C_{eq}}}$$

$$= \frac{1}{2\pi \sqrt{200 \times 10^{-6} \times 5 \times 10^{-8}}}$$

$$f = 50.33 \text{ KHz}$$

PROCEDURE :

1. Connections are given as per the circuit diagrams.
2. when an supply voltage V_{cc} is applied to the circuit, and note the corresponding output voltage.
3. the same procedure is repeated for the colpitt's oscillator.
4. The output waveform is obtained and noted.
5. A graph is drawn for the output waveforms of both Hartley and colpitt's oscillator.

RESULT :

Thus the Hartley and Colpitt's oscillators were designed and constructed and its output waveform were drawn.

Hartley Oscillator :

Theoretical Frequency = 1.59 KHz. Practical Freq = 1.33 KHz

Colpitt's Oscillator :

Theoretical Frequency = 50.33 KHz. Practical Freq = 50 KHz

AMPLITUDE (V)

COLPIT'S OSCILLATOR

SCALE

X-AXIS UNIT = 5 μ S

Y-AXIS UNIT = 0.65 V

Frequency = 50 KHz

