
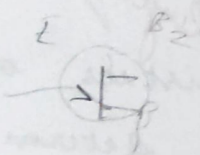


CIRCUIT DIAGRAM :

UTT:

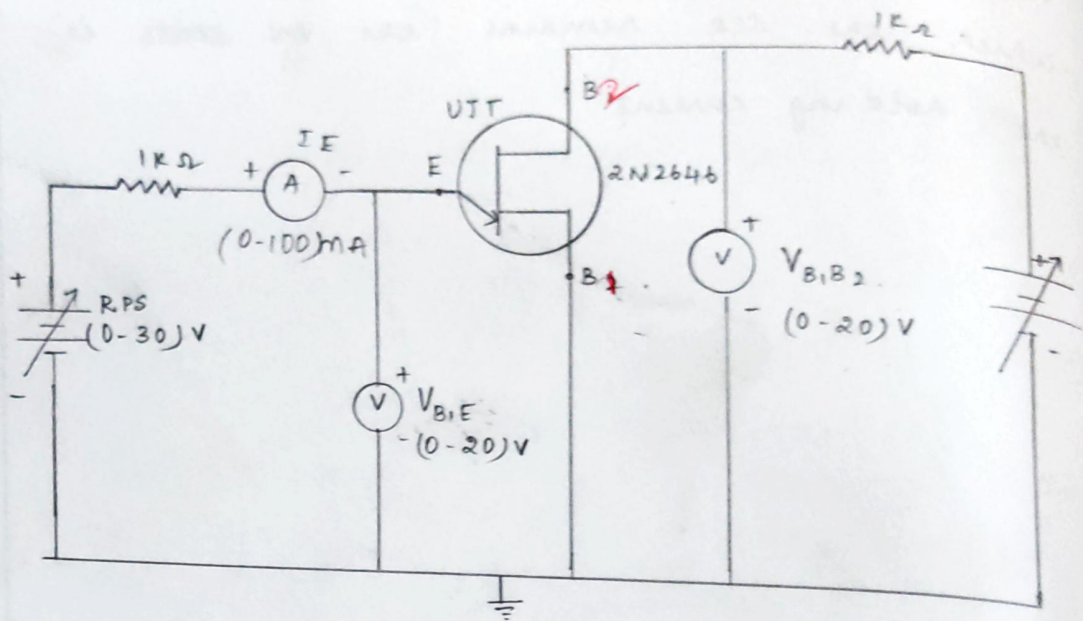

VI characteristic of UJT

ON 2000 100-0.5mA

ON 4000 100-0.5V



$$\eta_1 = \frac{V_P - V_V}{V_{BB}}$$

$$= \frac{3.29 - 1.47}{10}$$

$$\eta_1 = 0.36 A$$

$$\eta_2 = \frac{V_P - V_V}{V_{BB}}$$

$$= \frac{6.2 - 1.4}{10}$$

$$\eta_2 = 0.48 A$$

$$\eta = \frac{\eta_1 + \eta_2}{2}$$

$$= \frac{0.844}{2}$$

$$\eta = 0.42 (\text{no units})$$




b) CHARACTERISTICS OF UJT


AIM:

To observe the characteristics of uni-junction transistor and to calculate the intrinsic stand-off ratio (η).

APPARATUS REQUIRED:

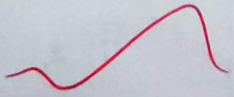SL NO.	APPARATUS NAME	TYPE / RANGE	QUANTITY
1.	Dual Regulated power supply (RPS)	(0-30)V	1
2.	Voltmeter	(0-20)V	2
3.	Ammeter	(0-100)mA	1
4.	Bread Board	-	1
5.	Uni Junction Transistor	2N2646	1
6.	Resistor	470 Ω	1
7.	connecting 	-	As required.

UTT

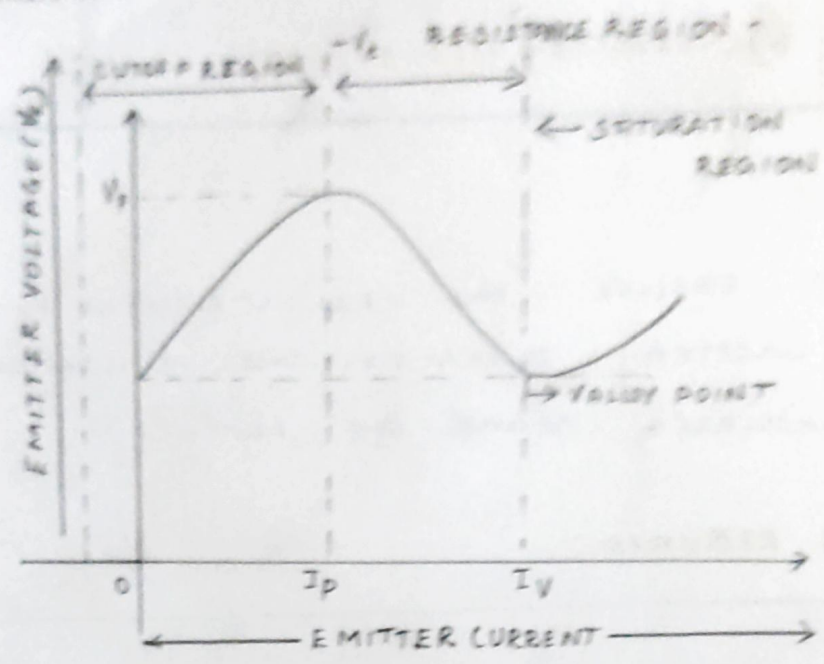

TABULATIONS :

$V_{BB} = 5V$		$V_{BB} = 10V$	
$V_{EB}(V)$	$I_E(mA)$	$V_{EB}(V)$	$I_E(mA)$
0.5	0	0.5	0
1	0	1	0
1.5	0	2	0
2	0	3	0
2.5	0	4	0
3	0	5	0
3.5	0	6	0
4.5	1.32	6.5	1.33
1.78	1.36	7.2	1.69
1.5	1.35	5.02	1.92
1.4	8.10	2.88	2.88
2.1	8.76	4.2	3.10
		1.91	6.24
		2	

FORMULA :

$$\text{Intrinsic stand-off ratio } (\eta) = \frac{V_p - V_D}{V_{BB}} .$$

V_p - Peak point voltage .

V_D - Diode cut-in-voltage .

V_{BB} - Voltage between base 1 and base 2 .

(i.e) Inter-base voltage .

PROCEDURE:

* connections are made as per the circuit diagram.

* Output voltage is fixed at a constant level and by varying input voltage corresponding emitter current values are noted down.

* This procedure is repeated for different values of output voltages.

* All the readings are tabulated and intrinsic stand-off ratio is calculated using $\eta = \frac{V_P - V_D}{V_{BB}}$.

* A graph is plotted between $V_{EE} + I_E$ for different values of V_{BE}



RESULT :

Thus the characteristics of uni-junction transistor was determined and intrinsic stand-off ratio (η) are determined.

(i.e) Intrinsic stand off
ratio (η) = 0.2

